Hamming encoder algorithm

06 October 2014 01:44

Iruth tab	ile							
Number	D3	D2	D1	D0	В0	B2	B4	В6
0	0	0	0	0	1	1	1	0
1	0	0	0	1	0	0	0	0
2	0	0	1	0	1	0	0	1
3	0	0	1	1	0	1	1	1
4	0	1	0	0	0	1	0	1
5	0	1	0	1	1	0	1	1
6	0	1	1	0	0	0	1	0
7	0	1	1	1	1	1	0	0
8	1	0	0	0	0	0	1	1
9	1	0	0	1	1	1	0	1
10	1	0	1	0	0	1	0	0
11	1	0	1	1	1	0	1	0
12	1	1	0	0	1	0	0	0
13	1	1	0	1	0	1	1	0
14	1	1	1	0	1	1	1	1
15	1	1	1	1	0	0	0	1

В0

D1D0\D3D2	00	01	11	10
00	1		1	
01		1		1
11		1		1
10	1		1	

Function

Function $out = \overline{D3} \cdot \overline{D2} \cdot \overline{D0} + \overline{D3} \cdot D2 \cdot D0 + D3 \cdot D2 \cdot \overline{D0} + D3 \cdot \overline{D2} \cdot D0$ $out = \overline{D3} \cdot (\overline{D2} \cdot \overline{D0} + D2 \cdot D0) + D3 \cdot (D2 \cdot \overline{D0} + \overline{D2} \cdot D0)$ $out = \overline{D3} \cdot (\overline{D2} \oplus \overline{D0}) + D3 \cdot (D2 \oplus D0)$

 $out = \overline{D0 \oplus D2 \oplus D3}$

B2

DZ.				
D1D0\D3D2	00	01	11	10
00	1	1		
01			1	1
11	1	1		
10			1	1

Function

 $out = \overline{D0 \oplus D1 \oplus D3}$

UT				
00	01	11	10	
1			1	
	1	1		
1			1	
	1	1		
	_	1 1	1 1	

Function

 $out = \overline{D0 \oplus D1 \oplus D2}$

ВО				
D1D0\D3D2	00	01	11	10
00		1		1
01		1		1
11	1		1	
10	1		1	

Function

 $out = D1 \oplus D2 \oplus D3$

Summary

Julilliary			
В7	D3		
В6	$D1 \oplus D2 \oplus D3$		
B5	D2		
B4	$\overline{D0 \oplus D1 \oplus D2}$		
В3	D1		
B2	$\overline{D0 \oplus D1 \oplus D3}$		
B1	D0		
В0	$\overline{D0 \oplus D2 \oplus D3}$		