ELEC2202 2013/14

D1 Design Completion Form

Name:
In July
bo 2hi

Username: yz39g13

_		
	Sequencer simulation shows correct functionality	7. T
	Whole system simulation shows correct functionality	B. H
	Sequencer for 4-bit multiplication implemented on MachXO2, goes through sequence of states, stops and displays READY	A
	4-bit adder implemented and shows correct functionality	The
	C,A,Q registers for 4-bit operation implemented and show correct functionality	KI
	Whole 4-bit system implemented and shows correct functionality	J. J.
	ADD and SHIFT combined in a single state	Of S
	Extension to 8 bits implemented and shows correct functionality	H.

Supervisor's signature_

Date 21/11/14

Formal report to be submitted through C-Bass/ECS front desk, by 16:00, one calendar week after the scheduled laboratory session.

Include a copy of this completion form with your formal report.