

## ELEC2202 Digital Systems and Communications

Introduction to design experiment D1  
CPLD implementation of a SHIFT-ADD multiplier



### D1

- Mark contributes 15% to the module's assessment
- You work and are assessed individually
- Time in lab is one full day, i.e. both lab sessions, am and pm.
- Formal report required for assessment
  - log book is not marked
  - progress is not marked in lab
  - preparation is your responsibility and is not marked in lab
  - However:
- In lab you need to fill in the Design Completion Form, get it signed by your supervisor and attach to your formal report
  - The Design Completion Form will be taken into account during assessment, so preparation and progress demonstrated in lab are important!

ELEC2202 Digital Systems and Communications D1- 2

### Preparation for D1

- You need to develop, test, and demonstrate a PLD implementation of a fairly complex sequential digital system, (a 4-bit sequential multiplier) using a MachXO2 CPLD.
- To assure success, before the lab:
  - develop your SystemVerilog code and testbenches for each module,
  - develop a testbench for the whole design
  - verify individual modules and whole design in Modelsim,
  - synthesise modules in Synplify.
- Devise a scheme to debounce the START button
  - Important as the internal clock of the CPLD is high, approx 25MHz.

ELEC2202 Digital Systems and Communications D1- 3

### Shift-and-add multiplication example

Multiply 7 x 5 in unsigned binary using the ADD & SHIFT algorithm:


111	M u l t i p l i c a n d
x 101	Q u a n t i p l i e r
111	(ADD 7, Q[0]= 1)
0000	(don' t ADD, Q[1] = 0)
111	(ADD 7 s h i f t e d b y 2 b i t s, Q[2]=1)
100011	(r e s u l t = 35)

ELEC2202 Digital Systems and Communications D1- 4
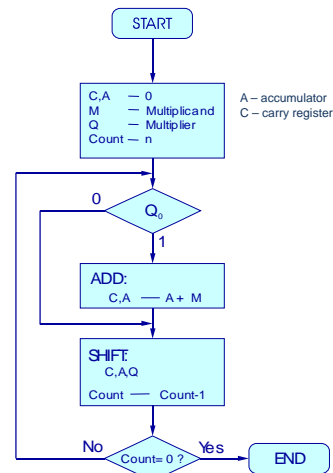
### Shift-and-add algorithm for n bits

```

      111 M
x   101 Q
-----
111000 A after ADD 1
011100 A after SHIFT 1
001110 A after SHIFT 2
carry 1000110 A after ADD 3
100011 A after SHIFT 3
  
```



ELEC2202 Digital Systems and Communications D1-5


### Same example cycle by cycle

M=	1	1	1	(M=7)	
C	0	0	0	1	0
A	0	0	0	0	0
Q	1	0	1	1	1
Initial Values					
ADD: A := A+M					
SHIFT (cycle 1)					
SHIFT (cycle 2)					
ADD: A := A+M					
SHIFT (cycle 3)					
A, Q =	0	1	0	0	0 1 1 = 35

Note: here the double length accumulator AQ shares storage with multiplier Q


ELEC2202 Digital Systems and Communications D1-6

### Hardware implementation

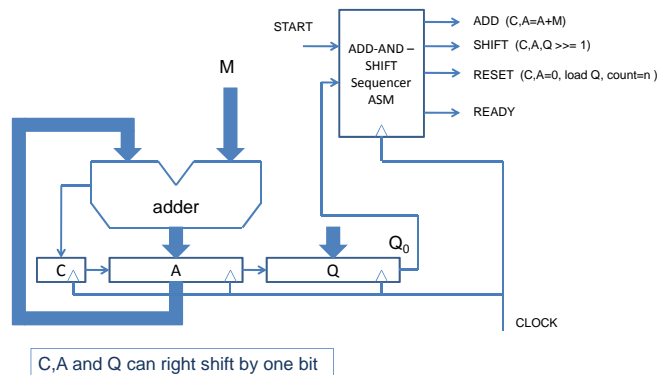


ELEC2202 Digital Systems and Communications D1-7

### Sequencer ASM chart

 

ELEC2202 Digital Systems and Communications D1-8
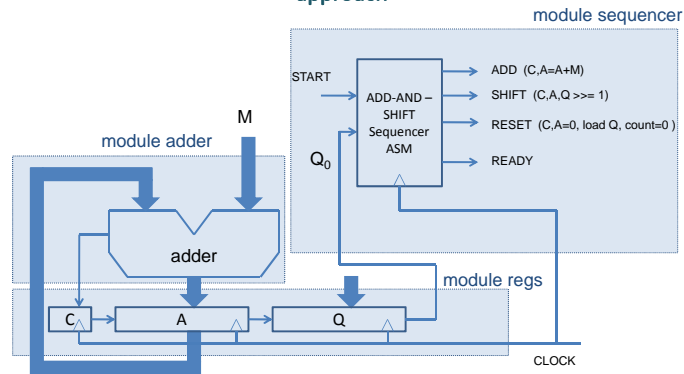
### CPLD implementation of an n-bit multiplier using hierarchical approach




ELEC2202 Digital Systems and Communications D1- 9

### Suggestions for further work

- Combine ADD and SHIFT in a single clock cycle
- Extend your multiplier design to more than 4 bits
  - MachXO will have plenty of room to spare
- Implement combinational array multiplier for comparison
  - Array multiplication is much faster than sequential shift-and-add
  - With only 4-bits an array multiplier might even be smaller than your sequential design!

ELEC2202 Digital Systems and Communications D1- 10

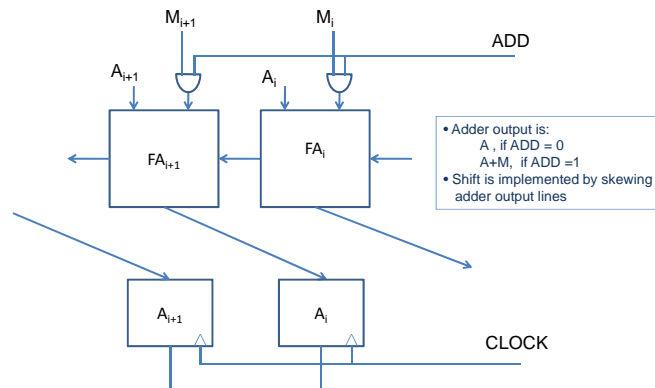
### How to combine ADD and SHIFT in single clock cycle



ELEC2202 Digital Systems and Communications D1- 11
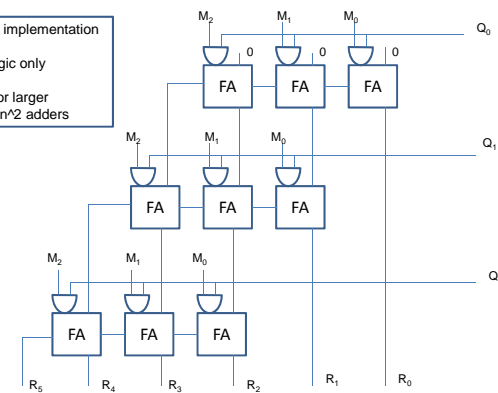
### Array multiplier Implements SHIFT and ADD in combinational logic

- Fastest multiplier implementation
- Combinational logic only
- Very expensive for larger numbers of bits:  $n^2$  adders



ELEC2202 Digital Systems and Communications D1- 12

### Coding in SystemVerilog

- SHIFT-AND-ADD sequencer is a standard state machine plus a cycle counter
- Adder is standard combinational logic
- C,A,Q registers are shift registers with parallel load
- Read D1 notes on the ELEC2014 notes page and PLD area on the labs pages for details specific to MachXO.

ELEC2202 Digital Systems and Communications D1- 13

### C,A,Q registers in SystemVerilog

```

module Regs(input logic clock, reset, add, shift, C,
            input logic[3:0] Qin, Sum, output logic[7:0] AQ);

    logic Creg; // MSB carry bit storage

    always_ff @ (posedge clock)
    if(reset) // clear C,A and load Q
    begin
        Creg <= 0;
        AQ[7:4] <= 0;
        AQ[3:0] <= Qin; // load multiplier into Q
    else if (add) // store Sum in C,A
    begin
        Creg <= C;
        AQ[7:4] <= Sum;
    end
    else if (shift) // shift A,Q
    begin
        // use concatenation to implement shift: Carry into MSB of A
        // and AQ by one bit to right: AQ[0] <= AQ[1], AQ[1] <= AQ[2]; ...
        // note also that Creg must be cleared
        {Creg,AQ} <= {1'b0,Creg,AQ[7:1]};
    end
end

endmodule

```

ELEC2202 Digital Systems and Communications D1- 14

### 4-bit adder in SystemVerilog

```

module Adder (input logic[3:0] A,M, output logic C, output logic [3:0] Sum);
    // Synplify can synthesise A+M, but output carry needs to be derived

    // 9-bit arithmetic addition allows to extract carry
    assign {C,Sum} = {1'b0,A} + {1'b0,M};

endmodule

```

ELEC2202 Digital Systems and Communications D1- 15

### General advice on coding and testing

- Write a separate testbench for each PLD
- Also write a testbench for whole design
- Synthesise each PLD and test separately using Digital Testbed
- Use a slow clock for testing but also demonstrate your design using a fast clock

ELEC2202 Digital Systems and Communications D1- 16

### Encapsulating module for whole design

```

module multiplier // for MachXO implementation – read MachXO lab notes
#(parameter n=4)
(input logic nPB, // active low push button, e.g. S1
 input logic nreset, output logic [7:0] leds);

// Instantiate the MachXO internal 25MHz oscillator
OSCC OSCC_INST (.OSC(fastclk));

logic shift,reset, C, start,pulse,clk;
logic [n-1:0] M,Q,sum;
logic[2*n-1:0] AQ;
//internal signals
logic C, reset, shift, add;

assign leds = ~AQ; // MachXO Mini Kit leds are active low

// module instances, note: cannot always use implicit mapping syntax here
adder A(AQ[7:4], .M(M), .C(C), .Sum(Sum)); // must use named mapping here
regs R(.); // named mapping equivalent: (.clock(clock), .reset(reset), ... etc.)
sequencer S(.clock(clock), .Q0(AQ[0]), ... etc. ) // use named mapping
endmodule

```

ELEC2202 Digital Systems and Communications D1- 17

### Testbench for whole design – simulation only

```

module TestMultiplier;

logic clock, C, start, ready, reset, shift, add;
logic [2:0] M,Qin, Sum;
logic [5:0] AQ;

// multiplier instance - can use implicit mapping syntax
multiplier m(.);

initial ... Specify your test waveforms here

....
endmodule

```

#### Notes:

- 1) Test whole design in Modelsim,
- 2) Also test each module separately in Modelsim and synthesise modules in Synplify Pro.

ELEC2202 Digital Systems and Communications D1- 18